

## MINISTRY EDUCATION, CULTURE, RESEARCH AND TECHNOLOGY UNIVERSITY COUNTRY JAKARTA FACULTY MATHEMATICS AND KNOWLEDGE KNOWLEDGE


NATURAL

## PRODI PHYSICS & EDUCATION **PHYSICS**


Campus A UNJ Rawamangun, Gd. Hasjim Asj'arie Lt. 5 Jl. Rawamangun Advance No. 1 Jakarta 13220 Tel. 021-29266285/29266284

| EXAM MIDDLE SEMESTER 118 |                               |  |
|--------------------------|-------------------------------|--|
| PHYSICS BASE II          |                               |  |
| Date and time            | Monday, 27 March 2023         |  |
| O'clock                  | 08.00-09.40 WIB               |  |
| Study Program            | Physics And Education Physics |  |
| Characteristic<br>Exam   | Closed book                   |  |
| Lecturer                 | Prof. Dr. I Made Astra,       |  |
|                          | M.ScDr. Umiatin, M.Si         |  |
|                          | Dr. Hadi Nasbey, M.Sc         |  |

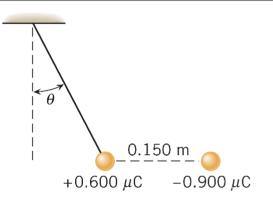
1. A insulator ball small with mass 8.00x 10<sup>-2</sup> kg And load electricity 0.600 µC hanged with a thread wire Which mass can ignored. A load -0.900 µC is held 0.150 m from the spherical insulator small And appropriate in adjacent right, so that the wire forms an angle  $\theta$  with vertical (see picture). Find (a) angle  $\theta$  And (b) voltage wire.



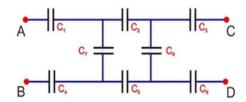2. Take note arrangement capacitor following: 3 capacitor on from left to right  $C_1 =$ 600 uF, C  $_2$  = 120 uF, and C  $_3$  = 240 uF, 3 bottom capacitors from left to right C  $_4$ = 200 uF, C  $_5$  = 240 uF and C  $_6$  = 300 uF and the 2 middle ones C  $_7$  left = 260 uF and right C  $_8$  = 80 uF . If a voltage of 100 V is applied between A and B, calculate the charge stored in each capacitor and electrical energy stored in Suite.



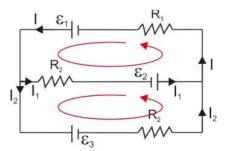3. Consider the following closed circuit. If the magnitude of E  $_1$  = 16 V, E  $_2$  = 8 V,  $E_3 = 10 \text{ Vand } R_1 = 12 \text{ ohms}, R_2 = 6 \text{ ohms}, \text{ and } R_3 = 6 \text{ ohms}.$  Calculate the magnitude of I, I<sub>1</sub> and I<sub>2</sub> And big energy electricity each minute on R<sub>1</sub>.



MINISTRY EDUCATION, CULTURE,
RESEARCH AND TECHNOLOGY
UNIVERSITY COUNTRY JAKARTA
FACULTY MATHEMATICS AND KNOWLEDGE KNOWLEDGE
NATURAL

## PRODI PHYSICS & EDUCATION PHYSICS

Campus A UNJ Rawamangun, Gd. Hasjim Asj'arie Lt. 5 Jl. Rawamangun Advance No. 1 Jakarta 13220 Tel. 021-29266285/29266284

| EXAM MIDDLE SEMESTER 118 |                               |  |
|--------------------------|-------------------------------|--|
| PHYSICS BASE II          |                               |  |
| Date and time            | Monday, 27 March 2023         |  |
| O'clock                  | 08.00-09.40 WIB               |  |
| Study Program            | Physics And Education Physics |  |
| Characteristic<br>Exam   | Closed book                   |  |
| Lecturer                 | Prof. Dr. I Made Astra,       |  |
|                          | M.ScDr. Umiatin, M.Si         |  |
|                          | Dr. Hadi Nasbey, M.Sc         |  |

4. Two wire segments as shown in the figure, have a current i  $_1$  = 0.4 A flowing through themsecond wire (bottom) with a radius of 5 cm and an angle of 180  $^{\circ}$  . On the first (top) wire segment carries current i  $_2$  = 2 i  $_1$  and the arc part of the circle with finger – finger 4 cm as well as corner 120  $^{\circ}$ . Second wire own center Which The sameat point P. Calculate the magnitude and direction of the magnetic field at P due to the two segments wire the.

